

Electrical Engineering Preparation Summary

Your Name

August 25, 2025

Contents

| | | |
|----------|--|----------|
| 1 | Introduction | 2 |
| 2 | Electrical Machines | 2 |
| 2.1 | Electromotive Force (EMF) | 2 |
| 2.2 | Radial Speed | 2 |
| 2.3 | Current Flow in the Circuit | 3 |
| 2.4 | Electromagnetic Torque | 3 |
| 2.5 | Determining Motor or Generator Operation | 4 |
| 3 | RLC Circuits | 5 |
| 3.1 | Resonance Curve (<i>la courbe de résonance</i>) | 5 |
| 3.2 | Impedance at Resonance in Series and Parallel RLC Circuits | 6 |
| 4 | Three-Phase Circuits | 6 |
| 4.1 | Line Current in a Delta (Triangular) System | 6 |
| 5 | Additional Notes | 7 |
| 5.1 | Lamps | 7 |

1 Introduction

This document provides a concise summary of key electrical engineering concepts focused on electrical machines, RLC circuits, three-phase circuits, and additional notes on lamps. It covers electromotive force (EMF), radial speed, current flow, electromagnetic torque, the resonance curve, impedance behavior in series and parallel RLC circuits, current relationships in three-phase delta systems, and characteristics of incandescent and fluorescent lamps to aid in preparation.

2 Electrical Machines

2.1 Electromotive Force (EMF)

Electromotive Force (EMF) is the voltage generated in a conductor moving through a magnetic field, such as in a generator or motor.

$$\text{Formula: } E = \frac{pN\Phi n}{a}$$

- **Parameters:**
 - E : Induced EMF (V).
 - p : Number of poles in the machine.
 - N : Number of conductors.
 - Φ : Magnetic flux in Wb per pole (Wb).
 - n : Rotational speed (rad s^{-1}).
 - a : Number of parallel paths in the winding.
- **Explanation:** The EMF is proportional to the number of poles, conductors, magnetic flux, and rotational speed, divided by the parallel paths. This is critical for understanding voltage generation in machines like generators.
- **Example:** A 4-pole generator with 100 conductors, a flux of 0.02 Wb, speed of 1200 rpm, and 2 parallel paths generates an EMF calculated by converting speed to radians per second (see below) and applying the formula.

2.2 Radial Speed

Radial Speed (or angular speed, ω) represents how fast a rotor spins in a rotating machine, measured in rad s^{-1} .

$$\text{Formula: } \omega = \frac{2\pi n}{60}$$

- **Parameters:**
 - ω : Angular speed (rad s^{-1}).
 - n : Rotational speed in revolutions per minute (RPM).

- **Simple Explanation:** This formula converts rotational speed from RPM to radians per second. One revolution equals 2π radians, and dividing by 60 adjusts for seconds in a minute. For example, at 1200 RPM:

$$\omega = \frac{2\pi \cdot 1200}{60} = 40\pi \approx 125.66 \text{ rad s}^{-1}.$$

- **Why It Matters:** Angular speed is used in EMF and torque calculations to determine how fast the magnetic field changes, affecting voltage and mechanical output.

2.3 Current Flow in the Circuit

Current Flow in a circuit (armature) of an electrical machine is determined by the difference between the EMF and the voltage across the circuit, accounting for the internal resistance.

$$\text{Formula: } I = \frac{E - V}{R}$$

- **Parameters:**

- I : Current flowing through the circuit (A).
- E : Electromotive force (EMF, V).
- V : Voltage across the circuit (V).
- R : Internal resistance of the circuit (Ω).

- **Explanation:** The current is driven by the difference between the generated EMF and the circuit's terminal voltage, divided by the internal resistance. The power consumed by the internal resistor is $P = I^2 R$, where I results from the voltage drop across the resistor, controlling current flow.

- **Example:** For an EMF of 100 V, a circuit voltage of 90 V, and an internal resistance of 2 Ω , the current is:

$$I = \frac{100 - 90}{2} = 5 \text{ A}.$$

The power consumed by the internal resistor is $P = 5^2 \cdot 2 = 50 \text{ W}$.

2.4 Electromagnetic Torque

Electromagnetic Torque (C) is the rotational force produced in an electrical machine, such as a motor, due to the interaction of current and magnetic flux.

$$\text{Formula: } C = \frac{E \cdot I}{\omega}$$

- **Parameters:**

- C : Torque (N m).
- E : Induced EMF (V).

- I : Current in the circuit (A).
- ω : Angular speed (rad s^{-1}).

- **Alternative Formula:**

$$\text{Formula: } C = \frac{p}{a} \cdot \frac{N \cdot \Phi \cdot I}{2\pi}$$

- p : Number of poles.
- a : Number of parallel paths.
- N : Number of conductors.
- Φ : Magnetic flux per pole (Wb).
- I : Current (A).

- **Explanation:** Torque is the mechanical output of an electrical machine, resulting from the interaction of the EMF and current, divided by angular speed in the first formula. The alternative formula expresses torque in terms of the machine's physical parameters, showing how the number of poles, conductors, flux, and current contribute to the rotational force. Both yield torque in N m.

- **Example:** For a machine with $E = 100 \text{ V}$, $I = 5 \text{ A}$, and $\omega = 125.66 \text{ rad s}^{-1}$ (from 1200 RPM), the torque is:

$$C = \frac{100 \cdot 5}{125.66} \approx 3.98 \text{ N m.}$$

Using the alternative formula, for $p = 4$, $a = 2$, $N = 100$, $\Phi = 0.02 \text{ Wb}$, and $I = 5 \text{ A}$:

$$C = \frac{4}{2} \cdot \frac{100 \cdot 0.02 \cdot 5}{2\pi} \approx 3.18 \text{ N m.}$$

(Note: Discrepancies may arise due to simplifying assumptions; verify with specific machine constants.)

2.5 Determining Motor or Generator Operation

Motor vs. Generator Operation can be determined by comparing the electromotive force (EMF) and the voltage across the armature (V) of the electrical machine.

- **Explanation:**

- **Generator Mode:** If the EMF (E) is greater than the armature voltage (V), i.e., $E > V$, the machine is operating as a generator. This is because the machine generates a higher voltage than the terminal voltage, driving current outward to supply power to an external load.
- **Motor Mode:** If the EMF (E) is less than the armature voltage (V), i.e., $E < V$, the machine is operating as a motor. In this case, an external voltage source supplies a higher voltage, driving current through the armature to produce mechanical work.

- The current flow formula $I = \frac{E-V}{R}$ determines the direction and magnitude of the current. In generator mode ($E > V$), current flows out of the machine (positive I). In motor mode ($E < V$), current flows into the machine (negative I).
- **Example:** For a machine with an internal resistance $R = 2\ \Omega$:
 - If $E = 100\ \text{V}$ and $V = 90\ \text{V}$, then $E > V$, and $I = \frac{100-90}{2} = 5\ \text{A}$. The positive current indicates generator operation, supplying power.
 - If $E = 90\ \text{V}$ and $V = 100\ \text{V}$, then $E < V$, and $I = \frac{90-100}{2} = -5\ \text{A}$. The negative current indicates motor operation, consuming power to produce mechanical work.
- **Why It Matters:** Comparing E and V allows quick identification of the machine's operating mode, critical for analyzing performance and efficiency in electrical systems.

3 RLC Circuits

3.1 Resonance Curve (*la courbe de résonance*)

Resonance Curve (*la courbe de résonance*) is a graph showing the variation of current intensity (or voltage across a circuit element) as a function of frequency (f) or angular frequency (ω) in a series RLC circuit.

- **Explanation:** In a series RLC circuit, consisting of a resistor (R), inductor (L), and capacitor (C), the resonance curve illustrates how the current or voltage across a component (e.g., resistor, inductor, or capacitor) changes with the input signal's frequency. At the resonance frequency, the inductive and capacitive reactances cancel each other out, resulting in maximum current (or minimum impedance) in the circuit. The resonance frequency occurs when:

$$\text{Formula: } \omega = \frac{1}{\sqrt{LC}},$$

where ω is the angular frequency (rad s^{-1}), L is inductance (H), and C is capacitance (F). The curve peaks at this frequency, showing a sharp increase in current, and decreases on either side, forming a bell-shaped graph.

- **Key Characteristics:**
 - The peak current occurs at the resonance frequency, where the circuit's impedance is purely resistive ($Z = R$).
 - The sharpness of the curve depends on the quality factor (Q), which is higher for lower resistance, indicating a narrower peak.
 - The resonance curve is critical for applications like tuning circuits in radios or filters in signal processing.
- **Example:** In a series RLC circuit with $R = 10\ \Omega$, $L = 0.1\ \text{H}$, and $C = 100\ \mu\text{F}$, the resonance angular frequency is:

$$\omega = \frac{1}{\sqrt{0.1 \cdot 100 \cdot 10^{-6}}} \approx 316.23\ \text{rad s}^{-1},$$

corresponding to a frequency of $f = \frac{\omega}{2\pi} \approx 50.33 \text{ Hz}$. Plotting the current versus frequency would show a peak at this value.

- **Why It Matters:** The resonance curve helps engineers analyze and design circuits for specific frequencies, optimizing performance in applications like communication systems and power electronics.

3.2 Impedance at Resonance in Series and Parallel RLC Circuits

Impedance at Resonance varies depending on whether the RLC circuit is configured in series or parallel.

- **Series RLC Circuit:** The impedance Z is minimal (equal to R) at resonance ($\omega = \omega_0$).
 - **Explanation:** At resonance, the reactances of the inductor and capacitor cancel out, leaving only the resistance R as the impedance. This results in maximum current flow.
- **Parallel RLC Circuit:** The impedance Z is maximal at resonance ($\omega = \omega_0$).
 - **Explanation:** At resonance, the parallel combination leads to a high effective impedance because the currents through the inductor and capacitor cancel, minimizing the total current drawn from the source.
- **Resonance Frequency:** For both configurations, $\omega_0 = \frac{1}{\sqrt{LC}}$.
- **Why It Matters:** Understanding impedance behavior at resonance is essential for designing circuits like filters, oscillators, and tuned amplifiers, where controlling current or voltage amplification is key.

4 Three-Phase Circuits

4.1 Line Current in a Delta (Triangular) System

Line Current in a Delta System relates the line current to the phase currents in a three-phase delta-connected system.

$$\text{Formula: } I_1 = J_1 - J_3$$

- **Phase Relationship:**

$$\text{Formula: } J_3 = J_1 \cdot e^{j \cdot \frac{2\pi}{3}} = J_1 \cdot e^{j \cdot \frac{-4\pi}{3}}$$

- **Parameters:**

- I_1 : Line current for phase 1 (A).
- J_1 : Phase current in branch 1 of the delta (A).
- J_3 : Phase current in branch 3 of the delta (A).

- **Explanation:** In a delta (triangular) configuration, the line current I_1 is the vector difference between the phase currents J_1 and J_3 . The phase currents in a three-phase system are 120 degrees ($\frac{2\pi}{3}$ radians) apart. The relationship $J_3 = J_1 \cdot e^{j \cdot \frac{2\pi}{3}}$ indicates that J_3 is phase-shifted from J_1 by 120° counterclockwise, while $J_3 = J_1 \cdot e^{j \cdot \frac{-4\pi}{3}}$ is equivalent, as $\frac{-4\pi}{3} = \frac{2\pi}{3} - 2\pi$ (a full cycle shift). Using the vector difference:

$$I_1 = J_1 - J_3 = J_1 - J_1 \cdot e^{j \cdot \frac{2\pi}{3}} = J_1(1 - e^{j \cdot \frac{2\pi}{3}}).$$

Simplifying, the magnitude of the line current is $\sqrt{3}$ times the phase current, and it leads or lags by 30°:

$$|I_1| = \sqrt{3}|J_1|.$$

- **Example:** If the phase current $J_1 = 10 \text{ A} \angle 0^\circ$, then:

$$J_3 = 10 \cdot e^{j \cdot \frac{2\pi}{3}} = 10 \angle 120^\circ.$$

The line current is:

$$I_1 = J_1 - J_3 = 10 \angle 0^\circ - 10 \angle 120^\circ.$$

Using phasor arithmetic:

$$I_1 = 10 - 10 \left(-\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = 10 + 5 - j5\sqrt{3} = 15 - j5\sqrt{3}.$$

The magnitude is:

$$|I_1| = \sqrt{15^2 + (5\sqrt{3})^2} = \sqrt{225 + 75} = \sqrt{300} \approx 17.32 \text{ A},$$

confirming $|I_1| = \sqrt{3} \cdot 10 \approx 17.32 \text{ A}$, with a phase angle of approximately 30° leading.

- **Why It Matters:** Understanding the relationship between line and phase currents in a delta system is crucial for designing and analyzing three-phase power systems, ensuring proper load balancing and efficient power distribution.

5 Additional Notes

5.1 Lamps

Lamps are common electrical loads with distinct electrical characteristics depending on their type.

- **Incandescent Lamps (Classical Filament):**

- **Characteristics:** Purely resistive because the filament heats up and glows to produce light.
- **Modeling:** In circuit analysis exercises, incandescent lamps are modeled as a resistor, resulting in a power factor of $\cos \phi = 1$, indicating no reactive power.

- **Why It Matters:** The purely resistive nature simplifies circuit calculations, as there is no phase difference between voltage and current.
- **Fluorescent Lamps or Discharge Lamps:**
 - **Characteristics:** Require a ballast (typically an inductor) to limit current flow due to their negative resistance behavior.
 - **Modeling:** In circuit analysis exercises, these lamps are modeled as inductive loads, resulting in a power factor of $\cos \phi < 1$, typically in the range of 0.6 to 0.8, indicating reactive power consumption.
 - **Why It Matters:** The inductive nature requires consideration of reactive power and power factor correction in circuit design to improve efficiency.