

# Electrical Engineering Preparation Summary

Your Name

August 25, 2025

## Contents

<b>1</b>	<b>Introduction</b>	<b>2</b>
<b>2</b>	<b>Electrical Machines</b>	<b>2</b>
2.1	Electromotive Force (EMF)	2
2.2	Angular Speed	2
2.3	Current Flow in the Circuit	3
2.4	Electromagnetic Torque	3
2.5	Determining Motor or Generator Operation	4
<b>3</b>	<b>RLC Circuits</b>	<b>5</b>
3.1	Resonance Curve ( <i>la courbe de résonance</i> )	5
3.2	Impedance at Resonance in Series and Parallel RLC Circuits	6
<b>4</b>	<b>Three-Phase Circuits</b>	<b>6</b>
4.1	Line Current in a Delta (Triangular) System	6
4.2	Power in Three-Phase Systems	7
4.3	Power Factor Correction in Three-Phase Systems	8
<b>5</b>	<b>Additional Notes</b>	<b>9</b>
5.1	Lamps	9

# 1 Introduction

This document provides a concise summary of key electrical engineering concepts focused on electrical machines, RLC circuits, three-phase circuits, and additional notes on lamps. It covers electromotive force (EMF), angular speed, current flow, electromagnetic torque, the resonance curve, impedance behavior in series and parallel RLC circuits, current relationships, power calculations, and power factor correction in three-phase systems, as well as characteristics of incandescent and fluorescent lamps to aid in preparation.

## 2 Electrical Machines

### 2.1 Electromotive Force (EMF)

**Electromotive Force (EMF)** is the voltage generated in a conductor moving through a magnetic field, such as in a generator or motor.

$$\text{Formula: } E = \frac{pN\Phi n}{a}$$

- **Parameters:**

- $E$ : Induced EMF (V).
- $p$ : Number of poles in the machine.
- $N$ : Number of conductors.
- $\Phi$ : Magnetic flux per pole (Wb).
- $n$ : Rotational speed ( $\text{rad s}^{-1}$ ).
- $a$ : Number of parallel paths in the winding.

- **Explanation:** The EMF is proportional to the number of poles, conductors, magnetic flux, and rotational speed, divided by the parallel paths. This is critical for understanding voltage generation in machines like generators.

- **Example:** A 4-pole generator with 100 conductors, a flux of 0.02 Wb, speed of 1200 rpm, and 2 parallel paths generates an EMF calculated by converting speed to radians per second (see below) and applying the formula.

### 2.2 Angular Speed

**Angular Speed** ( $\omega$ ) represents how fast a rotor spins in a rotating machine, measured in  $\text{rad s}^{-1}$ .

$$\text{Formula: } \omega = \frac{2\pi n}{60}$$

- **Parameters:**

- $\omega$ : Angular speed ( $\text{rad s}^{-1}$ ).

- $n$ : Rotational speed in revolutions per minute (RPM).
- **Simple Explanation:** This formula converts rotational speed from RPM to radians per second. One revolution equals  $2\pi$  radians, and dividing by 60 adjusts for seconds in a minute. For example, at 1200 RPM:

$$\omega = \frac{2\pi \cdot 1200}{60} = 40\pi \approx 125.66 \text{ rad s}^{-1}.$$

- **Why It Matters:** Angular speed is used in EMF and torque calculations to determine how fast the magnetic field changes, affecting voltage and mechanical output.

## 2.3 Current Flow in the Circuit

**Current Flow** in a circuit (armature) of an electrical machine is determined by the difference between the EMF and the voltage across the circuit, accounting for the internal resistance.

$$\text{Formula: } I = \frac{E - V}{R}$$

- **Parameters:**
  - $I$ : Current flowing through the circuit (A).
  - $E$ : Electromotive force (EMF, V).
  - $V$ : Voltage across the circuit (V).
  - $R$ : Internal resistance of the circuit ( $\Omega$ ).
- **Explanation:** The current is driven by the difference between the generated EMF and the circuit's terminal voltage, divided by the internal resistance. The power consumed by the internal resistor is  $P = I^2 R$ , where  $I$  results from the voltage drop across the resistor, controlling current flow.
- **Example:** For an EMF of 100 V, a circuit voltage of 90 V, and an internal resistance of  $2 \Omega$ , the current is:

$$I = \frac{100 - 90}{2} = 5 \text{ A}.$$

The power consumed by the internal resistor is  $P = 5^2 \cdot 2 = 50 \text{ W}$ .

## 2.4 Electromagnetic Torque

**Electromagnetic Torque** ( $C$ ) is the rotational force produced in an electrical machine, such as a motor, due to the interaction of current and magnetic flux.

$$\text{Formula: } C = \frac{E \cdot I}{\omega}$$

- **Parameters:**

- $C$ : Torque (N m).
- $E$ : Induced EMF (V).
- $I$ : Current in the circuit (A).
- $\omega$ : Angular speed ( $\text{rad s}^{-1}$ ).

- **Alternative Formula:**

$$\text{Formula: } C = \frac{p}{a} \cdot \frac{N \cdot \Phi \cdot I}{2\pi}$$

- $p$ : Number of poles.
  - $a$ : Number of parallel paths.
  - $N$ : Number of conductors.
  - $\Phi$ : Magnetic flux per pole (Wb).
  - $I$ : Current (A).
- **Explanation:** Torque is the mechanical output of an electrical machine, resulting from the interaction of the EMF and current, divided by angular speed in the first formula. The alternative formula expresses torque in terms of the machine's physical parameters, showing how the number of poles, conductors, flux, and current contribute to the rotational force. Both yield torque in N m.
  - **Example:** For a machine with  $E = 100 \text{ V}$ ,  $I = 5 \text{ A}$ , and  $\omega = 125.66 \text{ rad s}^{-1}$  (from 1200 RPM), the torque is:

$$C = \frac{100 \cdot 5}{125.66} \approx 3.98 \text{ N m.}$$

Using the alternative formula, for  $p = 4$ ,  $a = 2$ ,  $N = 100$ ,  $\Phi = 0.02 \text{ Wb}$ , and  $I = 5 \text{ A}$ :

$$C = \frac{4}{2} \cdot \frac{100 \cdot 0.02 \cdot 5}{2\pi} \approx 3.18 \text{ N m.}$$

- **Note:** Discrepancies between the two torque formulas may occur due to machine-specific constants (e.g., flux linkage or efficiency factors). Verify with manufacturer data for precise calculations.

## 2.5 Determining Motor or Generator Operation

**Motor vs. Generator Operation** can be determined by comparing the electromotive force (EMF) and the voltage across the armature ( $V$ ) of the electrical machine.

- **Explanation:**

- **Generator Mode:** If the EMF ( $E$ ) is greater than the armature voltage ( $V$ ), i.e.,  $E > V$ , the machine is operating as a generator. This is because the machine generates a higher voltage than the terminal voltage, driving current outward to supply power to an external load.

- **Motor Mode:** If the EMF ( $E$ ) is less than the armature voltage ( $V$ ), i.e.,  $E < V$ , the machine is operating as a motor. In this case, an external voltage source supplies a higher voltage, driving current through the armature to produce mechanical work.
- The current flow formula  $I = \frac{E-V}{R}$  determines the direction and magnitude of the current. In generator mode ( $E > V$ ), current flows out of the machine (positive  $I$ ). In motor mode ( $E < V$ ), current flows into the machine (negative  $I$ ).
- **Example:** For a machine with an internal resistance  $R = 2\ \Omega$ :
  - If  $E = 100\ \text{V}$  and  $V = 90\ \text{V}$ , then  $E > V$ , and  $I = \frac{100-90}{2} = 5\ \text{A}$ . The positive current indicates generator operation, supplying power.
  - If  $E = 90\ \text{V}$  and  $V = 100\ \text{V}$ , then  $E < V$ , and  $I = \frac{90-100}{2} = -5\ \text{A}$ . The negative current indicates motor operation, consuming power to produce mechanical work.
- **Why It Matters:** Comparing  $E$  and  $V$  allows quick identification of the machine's operating mode, critical for analyzing performance and efficiency in electrical systems.

### 3 RLC Circuits

#### 3.1 Resonance Curve (*la courbe de résonance*)

**Resonance Curve** (*la courbe de résonance*) is a graph showing the variation of current intensity (or voltage across a circuit element) as a function of frequency ( $f$ ) or angular frequency ( $\omega$ ) in a series RLC circuit.

- **Explanation:** In a series RLC circuit, consisting of a resistor ( $R$ ), inductor ( $L$ ), and capacitor ( $C$ ), the resonance curve illustrates how the current or voltage across a component (e.g., resistor, inductor, or capacitor) changes with the input signal's frequency. At the resonance frequency, the inductive and capacitive reactances cancel each other out, resulting in maximum current (or minimum impedance) in the circuit. The resonance frequency occurs when:

$$\text{Formula: } \omega = \frac{1}{\sqrt{LC}},$$

where  $\omega$  is the angular frequency ( $\text{rad s}^{-1}$ ),  $L$  is inductance (H), and  $C$  is capacitance (F). The curve peaks at this frequency, showing a sharp increase in current, and decreases on either side, forming a bell-shaped graph.

- **Key Characteristics:**
  - The peak current occurs at the resonance frequency, where the circuit's impedance is purely resistive ( $Z = R$ ).
  - The sharpness of the curve depends on the quality factor ( $Q$ ), which is higher for lower resistance, indicating a narrower peak.
  - The resonance curve is critical for applications like tuning circuits in radios or filters in signal processing.

- **Example:** In a series RLC circuit with  $R = 10\ \Omega$ ,  $L = 0.1\ \text{H}$ , and  $C = 100\ \mu\text{F}$ , the resonance angular frequency is:

$$\omega = \frac{1}{\sqrt{0.1 \cdot 100 \cdot 10^{-6}}} \approx 316.23\ \text{rad s}^{-1},$$

corresponding to a frequency of  $f = \frac{\omega}{2\pi} \approx 50.33\ \text{Hz}$ . Plotting the current versus frequency would show a peak at this value.

- **Why It Matters:** The resonance curve helps engineers analyze and design circuits for specific frequencies, optimizing performance in applications like communication systems and power electronics.

### 3.2 Impedance at Resonance in Series and Parallel RLC Circuits

**Impedance at Resonance** varies depending on whether the RLC circuit is configured in series or parallel.

- **Series RLC Circuit:** The impedance  $Z$  is minimal (equal to  $R$ ) at resonance ( $\omega = \omega_0$ ).
  - **Explanation:** At resonance, the reactances of the inductor and capacitor cancel out, leaving only the resistance  $R$  as the impedance. This results in maximum current flow.
- **Parallel RLC Circuit:** The impedance  $Z$  is maximal at resonance ( $\omega = \omega_0$ ).
  - **Explanation:** At resonance, the parallel combination results in high impedance, as inductor and capacitor currents cancel, minimizing total current from the source.
- **Resonance Frequency:** For both configurations,  $\omega_0 = \frac{1}{\sqrt{LC}}$ .
- **Why It Matters:** Understanding impedance behavior at resonance is essential for designing circuits like filters, oscillators, and tuned amplifiers, where controlling current or voltage amplification is key.

## 4 Three-Phase Circuits

### 4.1 Line Current in a Delta (Triangular) System

**Line Current in a Delta System** relates the line current to the phase currents in a three-phase delta-connected system.

$$\text{Formula: } I_1 = J_1 - J_3$$

- **Phase Relationship:**

$$\text{Formula: } J_3 = J_1 \cdot e^{j \cdot \frac{2\pi}{3}} = J_1 \cdot e^{j \cdot \frac{-4\pi}{3}}$$

- **Parameters:**

- $I_1$ : Line current for phase 1 (A).
- $J_1$ : Phase current in branch 1 of the delta (A).

–  $J_3$ : Phase current in branch 3 of the delta (A).

- **Explanation:** In a delta (triangular) configuration, the line current  $I_1$  is the vector difference between the phase currents  $J_1$  and  $J_3$ . The phase currents in a three-phase system are 120 degrees ( $\frac{2\pi}{3}$  radians) apart. The relationship  $J_3 = J_1 \cdot e^{j \cdot \frac{2\pi}{3}}$  indicates that  $J_3$  is phase-shifted from  $J_1$  by 120° counterclockwise, while  $J_3 = J_1 \cdot e^{j \cdot \frac{-4\pi}{3}}$  is equivalent, as  $\frac{-4\pi}{3} = \frac{2\pi}{3} - 2\pi$  (a full cycle shift). Using the vector difference:

$$I_1 = J_1 - J_3 = J_1 - J_1 \cdot e^{j \cdot \frac{2\pi}{3}} = J_1(1 - e^{j \cdot \frac{2\pi}{3}}).$$

Simplifying, the magnitude of the line current is  $\sqrt{3}$  times the phase current, and it leads or lags by 30°:

$$|I_1| = \sqrt{3}|J_1|.$$

- **Example:** If the phase current  $J_1 = 10 \text{ A} \angle 0^\circ$ , then:

$$J_3 = 10 \cdot e^{j \cdot \frac{2\pi}{3}} = 10 \angle 120^\circ.$$

The line current is:

$$I_1 = J_1 - J_3 = 10 \angle 0^\circ - 10 \angle 120^\circ.$$

Using phasor arithmetic:

$$I_1 = 10 - 10 \left( -\frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = 10 + 5 - j5\sqrt{3} = 15 - j5\sqrt{3}.$$

The magnitude is:

$$|I_1| = \sqrt{15^2 + (5\sqrt{3})^2} = \sqrt{225 + 75} = \sqrt{300} \approx 17.32 \text{ A},$$

confirming  $|I_1| = \sqrt{3} \cdot 10 \approx 17.32 \text{ A}$ , with a phase angle of approximately 30° leading.

- **Why It Matters:** Understanding the relationship between line and phase currents in a delta system is crucial for designing and analyzing three-phase power systems, ensuring proper load balancing and efficient power distribution.

## 4.2 Power in Three-Phase Systems

**Power in Three-Phase Systems** includes active, reactive, and apparent power, defined as:

$$\text{Formula: } P = \sqrt{3}V_L I_L \cos \phi, \quad Q = \sqrt{3}V_L I_L \sin \phi, \quad S = \sqrt{3}V_L I_L,$$

where  $P$  is active power (W),  $Q$  is reactive power (VAR),  $S$  is apparent power (VA),  $V_L$  is line voltage (V),  $I_L$  is line current (A), and  $\cos \phi$  is the power factor. Active power depends on  $\cos \phi$ , reactive power on  $\sin \phi$ , and apparent power has no trigonometric term.

### 4.3 Power Factor Correction in Three-Phase Systems

**Power Factor Correction** involves adding capacitors to reduce reactive power and improve the power factor in three-phase systems.

- **Initial Reactive Power:**

$$\text{Formula: } Q_1 = P \cdot \tan \phi_1$$

where  $Q_1$  is the initial reactive power (VAR),  $P$  is the active power (W), and  $\phi_1$  is the initial power factor angle.

- **Desired Final Reactive Power:**

$$\text{Formula: } Q_2 = P \cdot \tan \phi_2$$

where  $Q_2$  is the desired reactive power (VAR) after correction, and  $\phi_2$  is the desired power factor angle.

- **Reactive Power to be Compensated by Capacitors:**

$$\text{Formula: } Q_c = Q_1 - Q_2 = P(\tan \phi_1 - \tan \phi_2)$$

where  $Q_c$  is the reactive power provided by capacitors (VAR).

- **Origin of  $Q_c$ :** The reactive power  $Q_c$  represents the amount of reactive power that capacitors must supply to reduce the initial reactive power  $Q_1$  to the desired level  $Q_2$ , thereby improving the power factor from  $\cos \phi_1$  to  $\cos \phi_2$ . This is necessary because inductive loads (e.g., motors) consume reactive power, leading to a low power factor. Capacitors provide capacitive reactive power (opposite in sign to inductive reactive power), reducing the net reactive power demand on the system and improving efficiency.

- **Capacitor Sizing for Three-Phase Systems:**

- **Star (Y) Connection:**

$$\text{Formula: } Q_c = 3 \cdot U^2 \cdot \omega \cdot C$$

where  $Q_c$  is the reactive power (VAR),  $U$  is the phase-to-neutral voltage (V),  $\omega = 2\pi f$  is the angular frequency ( $\text{rad s}^{-1}$ ),  $f$  is the frequency (Hz), and  $C$  is the capacitance per phase (F). The capacitance is:

$$\text{Formula: } C = \frac{Q_c}{3 \cdot U^2 \cdot \omega}$$

- **Delta ( $\Delta$ ) Connection:**

$$\text{Formula: } Q_c = 3 \cdot U^2 \cdot \omega \cdot C$$

where  $U$  is the line-to-line voltage (V). The capacitance is:

$$\text{Formula: } C = \frac{Q_c}{3 \cdot U^2 \cdot \omega}$$



- **Clarification:** The formula for  $Q_c$  is the same for both star and delta connections, but the voltage  $U$  differs. In a star connection,  $U$  is the phase-to-neutral voltage ( $V_L/\sqrt{3}$ ), while in a delta connection,  $U$  is the line-to-line voltage ( $V_L$ ). This affects the capacitance value required for the same  $Q_c$ .
- **Example:** For a three-phase system with active power  $P = 100$  kW, initial power factor  $\cos \phi_1 = 0.8$  ( $\tan \phi_1 = 0.75$ ), desired power factor  $\cos \phi_2 = 0.95$  ( $\tan \phi_2 = 0.3287$ ), line voltage  $V_L = 400$  V, and frequency  $f = 50$  Hz:

$$Q_1 = 100 \cdot 0.75 = 75 \text{ kVAR}, \quad Q_2 = 100 \cdot 0.3287 = 32.87 \text{ kVAR},$$

$$Q_c = 75 - 32.87 = 42.13 \text{ kVAR}.$$

For a star connection,  $U = \frac{400}{\sqrt{3}} \approx 230.94$  V,  $\omega = 2\pi \cdot 50 \approx 314.16$  rad s<sup>-1</sup>:

$$C = \frac{42.13 \cdot 10^3}{3 \cdot 230.94^2 \cdot 314.16} \approx 879.6 \text{ } \mu\text{F per phase}.$$

For a delta connection,  $U = 400$  V:

$$C = \frac{42.13 \cdot 10^3}{3 \cdot 400^2 \cdot 314.16} \approx 279.2 \text{ } \mu\text{F per phase}.$$

- **Why It Matters:** Power factor correction reduces reactive power demand, lowers energy losses, and improves system efficiency, particularly in three-phase systems with inductive loads like motors.

## 5 Additional Notes

### 5.1 Lamps

**Lamps** are common electrical loads with distinct electrical characteristics depending on their type.

- **Incandescent Lamps (Classical Filament):**
  - **Characteristics:** Purely resistive because the filament heats up and glows to produce light.
  - **Modeling:** In circuit analysis exercises, incandescent lamps are modeled as a resistor, resulting in a power factor of  $\cos \phi = 1$ , indicating no reactive power.
  - **Why It Matters:** The purely resistive nature simplifies circuit calculations, as there is no phase difference between voltage and current.
- **Fluorescent Lamps or Discharge Lamps:**
  - **Characteristics:** Require a ballast (typically an inductor) to limit current flow due to their negative resistance behavior.
  - **Modeling:** In circuit analysis exercises, these lamps are modeled as inductive loads, resulting in a power factor of  $\cos \phi < 1$ , typically in the range of 0.6 to 0.8, indicating reactive power consumption.
  - **Why It Matters:** The inductive nature requires consideration of reactive power and power factor correction in circuit design to improve efficiency.